

Statement of Objectives:

- ① To implement multi-loops electrical circuits.
- ② To acquire an understanding of the conceptual meanings of the loop and junction.
- ③ To justify both kirchoff's junction rule and loop rule.
- ④ To apply both rules to multi-loop electrical circuits.

Background and Summary:

a) Brief Description of Theory:

- kirchoff's law is used to analyze complex circuits
- Junction (or Branchpoint) The term refers to any
- Loop :- The term refers to any closed path of a circuit such that the point you start with is also the point you end up with
- Junction Rule : Algebraic sum of all the currents entering and leaving any branchpoint in a circuit is equal to zero,
- Loop Rule : Algebraic sum of all potential diff. around a loop in a circuit is equal to zero $\sum \mathcal{E}_i - \sum I_i R_i = 0$

★ To apply the junction rule:

- 1) choose (B.P)
- 2) set the direction of the current
- 3) Apply the Junction rule $\sum I_i = 0$

★ To apply the loop rule:

- 1) $(-Ir)$
- 2) $(+\mathcal{E})$

Brief Description of Experiment and Procedure:

Part I: Two loop circuit with one voltage source:

1) connect the circuit for given resistors.

2) Measure the equivalent resistance R_{eq} with the power supply disconnected.

3) Measure the current through each resistor as I_1, I_2, I_3, I_4 and measure the equivalent current I_{eq} too.

this is not background

A We are going to measure the current passing through each resistor, and the voltage across each resistors then verify the Junction rule and loop rule.

① adjust the voltage to 10v.

② connect the circuit as shown in figure (1).

③ Measure I_1, I_2, I_3, I_4 and I_{eq} .

④ prove the junction Rule at point E and B.


⑤ measure the voltage V_1, V_2, V_3, V_4

Methodology: ⑥ Prove the loop rule at loops AB EF, BCDE and ACDF


a) List of Equipment:

- 1) Analog wires.
- 2) wires.
- 3) Resistors: $470 \Omega, 1k \Omega, 390 \Omega, 560 \Omega,$
- 4) Multimeter.

Diagrams of the Experimental Setup:

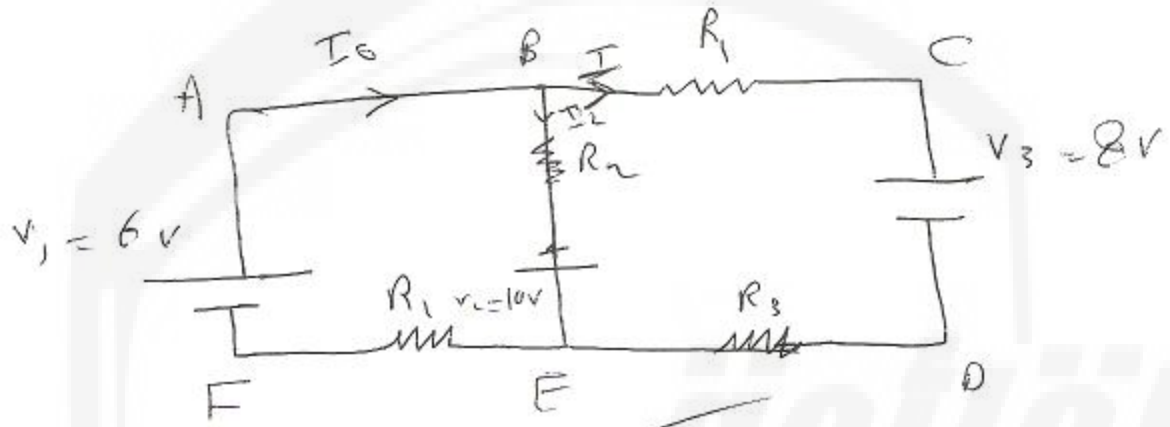

Fig(1)

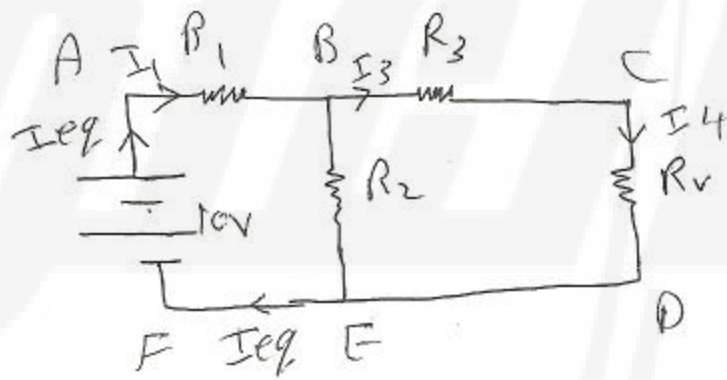

Fig(2)

c) Detailed Description of the Experimental Procedures:

part I: Two loop circuit with one voltage source =

1) Using the given four resistors ($R_1 = 560 \Omega$, $R_2 = 1 \text{ k}\Omega$, $R_3 = 470 \Omega$, $R_4 = 390 \Omega$), connect the circuit as show in figure 2.

2) Measure the equivalent resistance R_{eq} with the power supply disconnected. Record the data in table (1).

3) Measure the current through each resistors as I_1, I_2, I_3, I_4 and measure the equivalent current I_{eq} too. Record the data in table (1).

* We are going to measure the current passing through each resistor, and the voltage across each resistor, then verify the junction rule and loop rule.

~~for part II?~~

a) Statement of Error Sources:

- 1) Wrong in Reading
- 2) wrong in connection.
- 3) The Voltmeter giving wrong numbers.
- 4) The difference between calculating measured device
- 5) Fixed wires connection may cause this difference.

Data and Analysis of Results

a) Data tables, Sample calculations, and Error Analysis:

* Verify the junction B&E

For B.p (B)

$$I_1 = 9.71, (I_2 + I_3) = 4.51 + 5.20 = 9.71 \text{ (mA)}$$

therefore, $I_1 \approx I_2 + I_3$

For B.p (E)

$$I_2 + I_4 = 4.51 + 5.21 = 9.72$$

therefore, $I_2 + I_4 = 9.72 \approx I_{eq} \text{ (mA)}$

Is the junction rule verified, yes!

Verify the loop rule ABEFA & BCDEB

For the loop ABEFA, calculate

$$I_1 R_1 = \cancel{5.35 \times 10^3} (9.71) (551 \times 10^3) = 5.35$$

$$I_2 R_2 = 4.51 (988 \times 10^3) = 4.455$$

$$+ \mathcal{E} - I_1 R_1 - I_2 R_2 = 10 - 9.71 (551 \times 10^3) - 4.51 (988) \times 10^3 = 0.125 \approx 0$$

For the loop BCDEB

$$I_2 R_2 = 4.455, I_3 R_3 = 2.418, I_4 R_4 = 2.01$$

$$+ I_2 R_2 - I_3 R_3 - I_4 R_4 = 0.027 \approx 0$$

Is the loop rule verified, yes!

little? -0.25
Data table

Req (A)	Ieq (mA)	I1 (mA)	I2 (mA)	I3 (mA)	I4 (mA)
1009	9.72	9.71	4.51	5.20	5.21

Discussion and Conclusions:

a) Statement of Results and Comparison with Accepted Values:

for (B.p) F 8

$$I_{eq} = 9.72 \text{ (mA)}$$

$$+ \mathcal{E} - I_1 R_1 - I_2 R_2 = 0.195 \approx 0$$

for the loop BCDEB

$$I_2 R_2 - I_3 R_3 - I_4 R_4 = 0.027 \approx 0$$

$$\mathcal{E}_i = 0$$

$$\mathcal{E}_{vi} = 0$$

$$I_1 = 9.71 \text{ mA}$$

$$I_2 + I_3 = 9.71$$

$$I_1 - I_2 - I_3 = 0$$

$$I_{eq} = 9.72 \text{ (mA)}$$

$$I_2 + I_4 = 9.72$$

$$I_{eq} - I_2 - I_4 = 0$$

b) Discussion of Possible Methods to Reduce Uncertainties:

- 1) writing the right reading.
- 2) making the right connections.
- 3) The Voltmeter giving the reading.

c) Statement of General Conclusion:

* Kirchhoff's law :

* Junction :- The term refers to any point where three or more circuit elements meet.

* Loop :- The ~~term~~ term refers to any closed path of a circuit such that the point you start with is also the point you end up with.

* Reference :
Laboratory Manual & General Phys. lab II
phy. 107 & 127.