

Statement of Objectives:

- 1) To study charging and discharging process through capacitors.
- 2) To determine the time constant τ of an RC-circuit.

Background and Summary:

a) Brief Description of Theory:

* charging a capacitor :

The electrical charge Q of the capacitor at any given time t is equal to: $Q = C\varepsilon(1 - e^{-\frac{t}{RC}})$

* the voltage across the capacitor V_c : $V_c = \varepsilon(1 - e^{-\frac{t}{RC}})$

* At a specific value of time $t = \tau = RC$: $V_c = \varepsilon(1 - e^{-1})$

or $V_c = 0.63\varepsilon$

* The current: in the circuit at a given time t is given as

$$i = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$

* power relation :-

instantaneous rate at which the battery delivers energy to the circuit: $P\varepsilon = i\varepsilon$.

* Discharging a capacitor :-

* The electrical Q of a discharging capacitor at any given time, $Q = C\varepsilon e^{-\frac{t}{RC}}$

* the voltage across the capacitor V_c : $V_c = \varepsilon e^{-\frac{t}{RC}}$

* At time $t = \tau = RC$

$$V_c = \varepsilon e^{-1}$$

$$V_c = 0.37\varepsilon$$

the current i in the circuit

$$i = \frac{\varepsilon}{R} e^{-\frac{t}{RC}}$$

2

b) Brief Description of Experiment and Procedure:

We are going to measure the (t) For different value of $F (V)$ in both process charge.

in the other side of the experiment we are going to connect and turn the power supply to record the time then repeat the steps to calculate the bar, Finally plot the graph. V_c vs t_{avg} . and calculate τ and C




Methodology:

a) List of Equipment:


- * Electronic design experimentor.
- * 220 k Ω resistor.
- * 470 μF capacitor.
- * Multimeter.
- * Stop watch.
- * Connection wires.



b) Diagrams of the Experimental Setup:

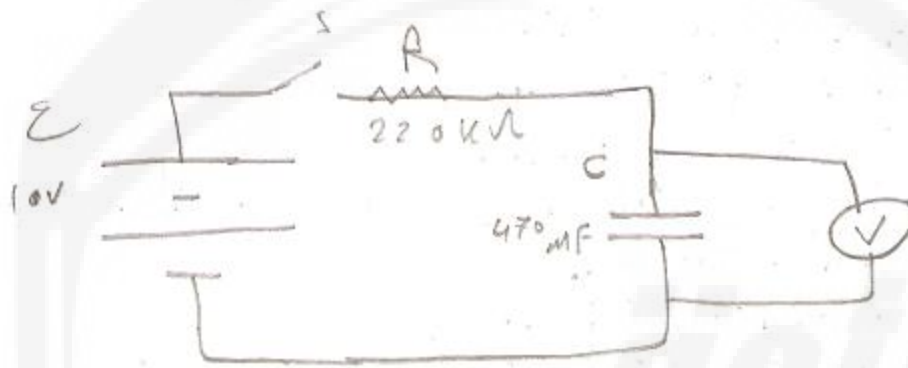

→ Figure (1)

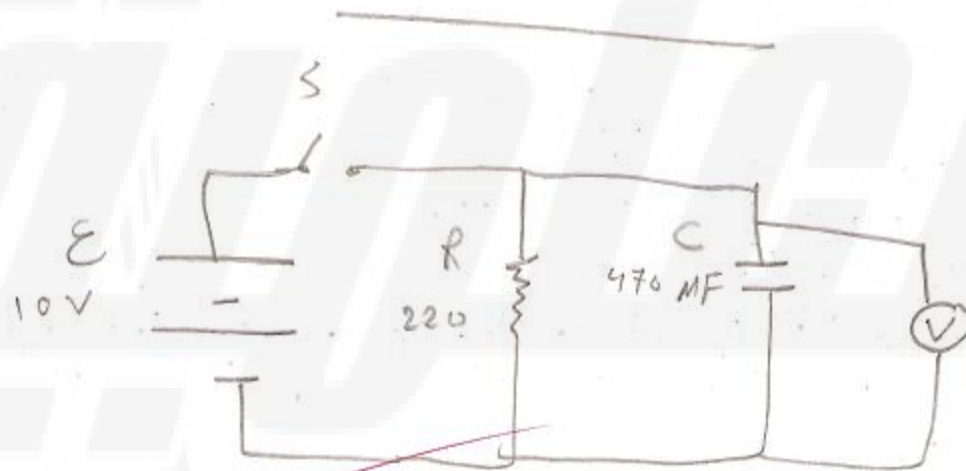

✓ Figure (2)

c) Detailed Description of the Experimental Procedures:

* part 1: Charging a capacitor (voltage V vs time):

- 1) Connect the circuit.
- 2) Turn on the power supply.
- 3) short out the capacitor
- 4) Close the switch S , and reset the stop watch.
- 5) record the time t_1
- 6) reset the stop watch.
- 7) repeat steps above for time corresponding
- 8) Calculate the average time t_{avg} .
- 9) plot a graph V vs t_{avg} .

* part 3: Discharging a capacitor (voltage V vs time)

- 1) Connected the circuit.
- 2) Turn on the power supply.
- 3) close the switch.
- 4) Start the stopwatch and open the switch S .
- 5) Corresponding to integer values of V_c according to table 3.
- 6) reset the stopwatch.
- 7) Repeat steps above for time
- 8) Calculate the average time t_{avg} .
- 9) Plot a graph for V_c vs t_{avg} .

d) Statement of Error Sources:

- 1) Wrong in Reading numbers.
- 2) Wrong in connections.
- 3) The stop watch may giving a wrong number.
- 4) The capacitor could not has charge before starting charging process.

Data and Analysis of Results

a) Data tables, Sample calculations, and Error Analysis:

table (1)
Capacitor voltage versus
time of charging capacitor

Data table

v _c (v)	t ₁ (s)	t ₂ (s)	tar = $\frac{t_1 + t_2}{2}$ (s)
0	0	0	0
1	11.97	12.19	12.08
2	24.75	24.82	24.785
3	39.5	39.63	39.56
4	56.66	56.75	56.70
5	1.17.26	1.17.28	77.265
6	1.43.67	1.42.78	102.925
7	2.18.07	2.16.78	187.74
8	3.10.97	3.07.97	199.47

6

table (2) ←
Capacitor voltage versus time of
discharging capacitor
Data table

V_c (V)	t_1 (s)	t_2 (s)	t_{av} (s)
10	0	0	0
9	11.11	11.69	11.4
8	23.58	23.97	23.77
7	38.17	37.92	38.04
6	54.49	54.31	54.4
5	114.05	114.13	114.09
4	139.05	137.95	137.95
3	209.33	208.72	209.025
2	254.05	253.57	253.81

→ Time constant (T)
from the graph

$$T = RC, \quad T = 115$$

$$R = 220 \times 10^3 \Omega$$

$$C = \frac{T}{R} = \frac{115}{220 \times 10^3} \\ = 5.2 \times 10^{-4} \text{ F}$$

* capacitance C (from
the graph)

Data table

--

Discussion and Conclusions:

a) Statement of Results and Comparison with Accepted Values:

- From first graph

$$I = Rc \text{ when } R = 220 \times 10^3$$

$$c = \frac{5.1 \times 10^{-4}}{220 \times 10^3} = 2.3 \times 10^{-9}$$

$$\text{error} = \frac{470 \times 10^{-6} - 2.3 \times 10^{-9}}{470 \times 10^{-6}} \times 100$$

$$= 0.999 \%$$

From the second graph

$$I = Rc \text{ when } R = 220 \times 10^3$$

$$c = \frac{5.2 \times 10^{-4}}{220 \times 10^3} = 2.3 \times 10^{-9}$$

$$\text{error} = \frac{470 \times 10^{-6} - 2.3 \times 10^{-9}}{470 \times 10^{-6}} \times 100$$

$$= 0.999 \%$$

b) Discussion of Possible Methods to Reduce Uncertainties:

1) Writing the right number

2) making the right connection.

3) The stopwatch giving the Readings

c) Statement of General Conclusion:

* In charging a capacitor a resistor is usually connected in series.

* In discharging a capacitor a resistor is usually connected in parallel

* The power conservation

$$P_E = P_R + P_C.$$

* Reference *

Laboratory Manual

General physics Lab II

Phys. 107 & 127

4

Graph (7)
charging Table (2) ⑨


units? \rightarrow 0.25

$$T = RC$$

$$R = 220 \times 10^3 \Omega$$

$$C = \frac{T}{R} = \frac{113}{220 \times 10^3}$$

$$= 5.1 \times 10^{-4} F$$

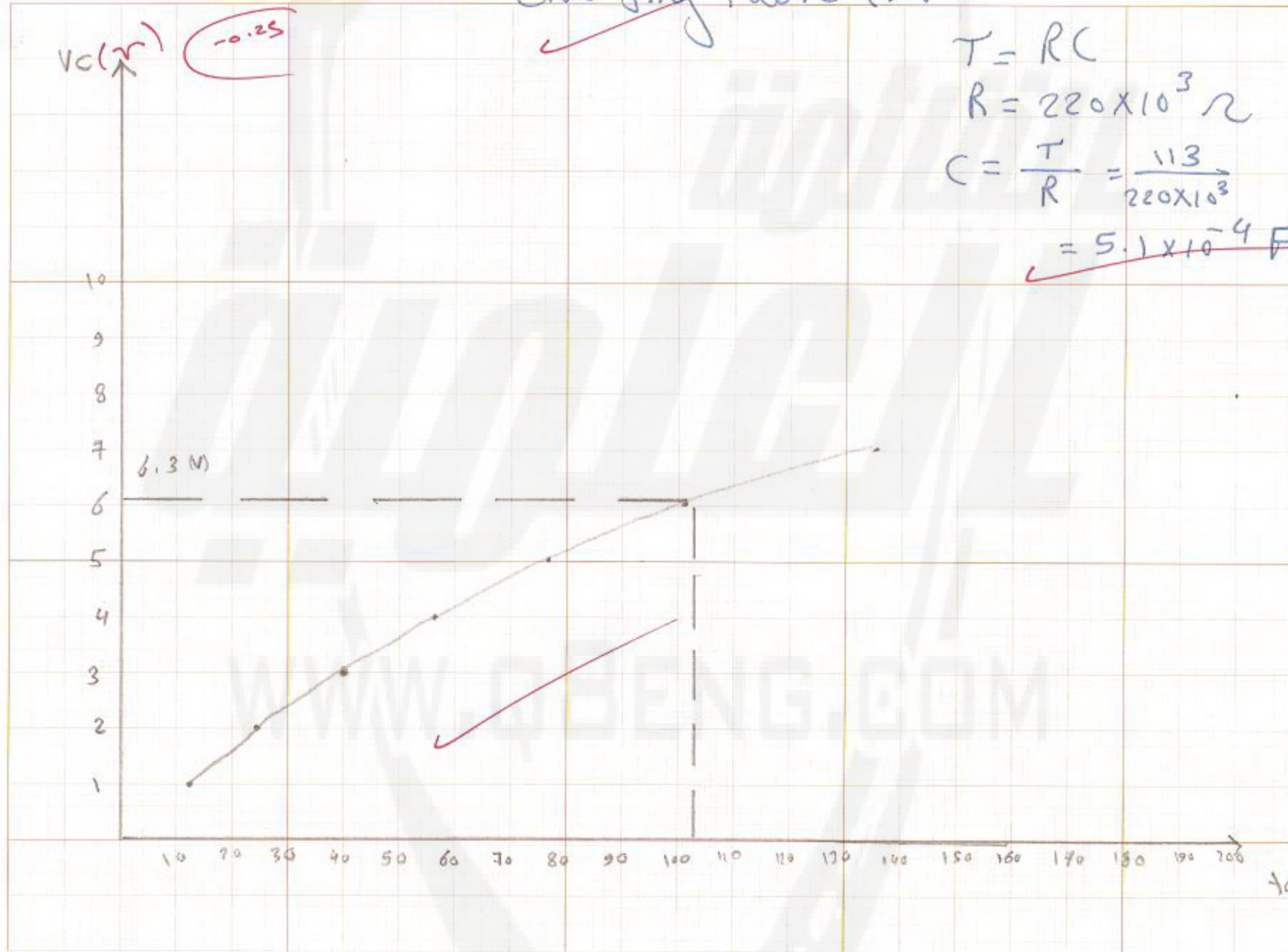

Scale 0.25

Graph (2) Discharging Table (3)

10

$$T = RC$$

$$R = 220 \times 10^3 \Omega$$

$$C = \frac{T}{R} = \frac{115}{220 \times 10^3} = 5.2 \times 10^{-4} F$$

